

Sequential Circuits

And Finite State Machines


Lab 1 checkoff due tomorrow (9/27)

Lab 2 due on Thu (9/28)

Quiz 1 happening on 10/5

Something We Cannot Build (Yet)

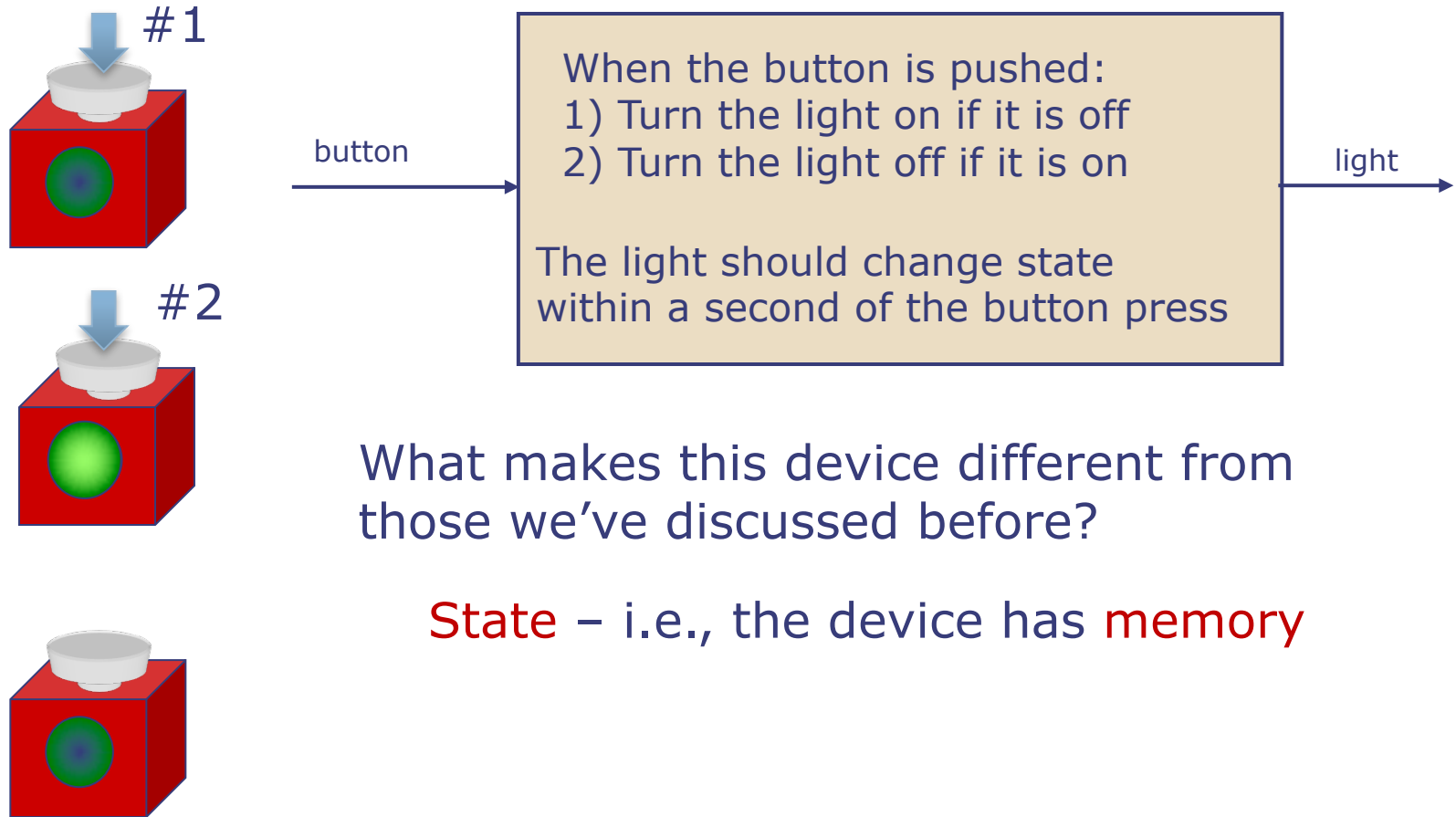
What if you were given the following design specification:



What makes this device different from those we've discussed before?

State – i.e., the device has **memory**

Sequential Circuits

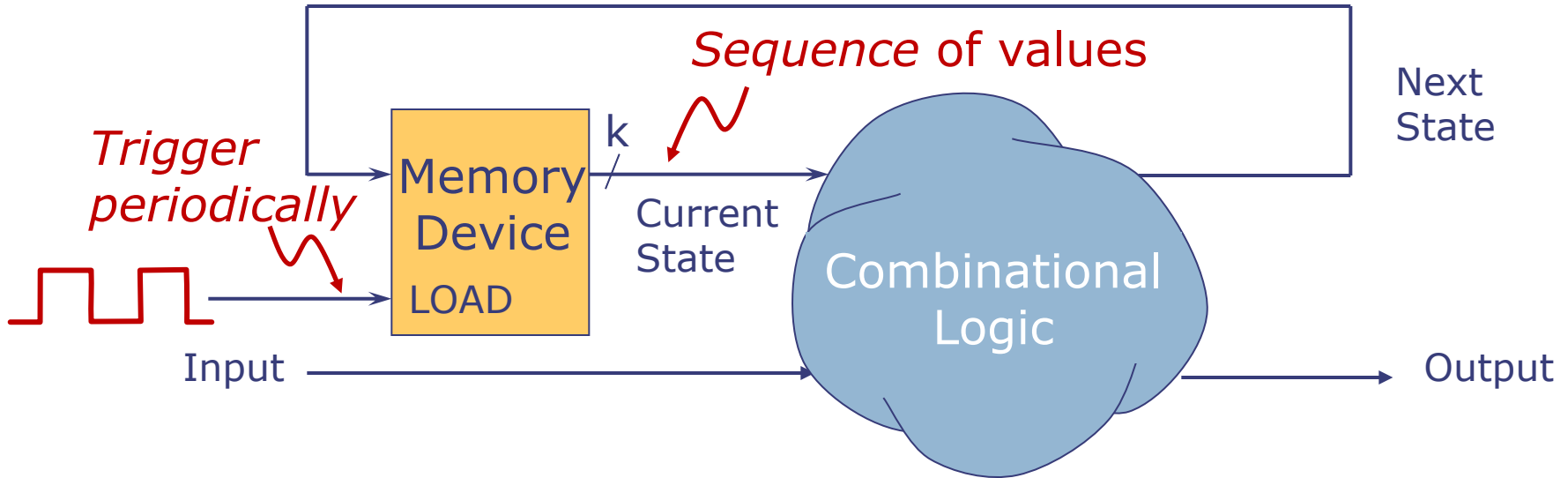


Sequential circuits contain digital memory and combinational logic

- Memory stores **current state**
- Combinational logic computes:
 - **Next state** (from input + current state)
 - **Output** bits (from input + current state)
- State changes on LOAD control input


Need
loadable
memory

Memory: Using Feedback

 Idea: use **feedback** to maintain storage indefinitely.
Our logic gates are built to restore marginal signal levels, so noise shouldn't be a problem!



Result: a **bistable storage element**

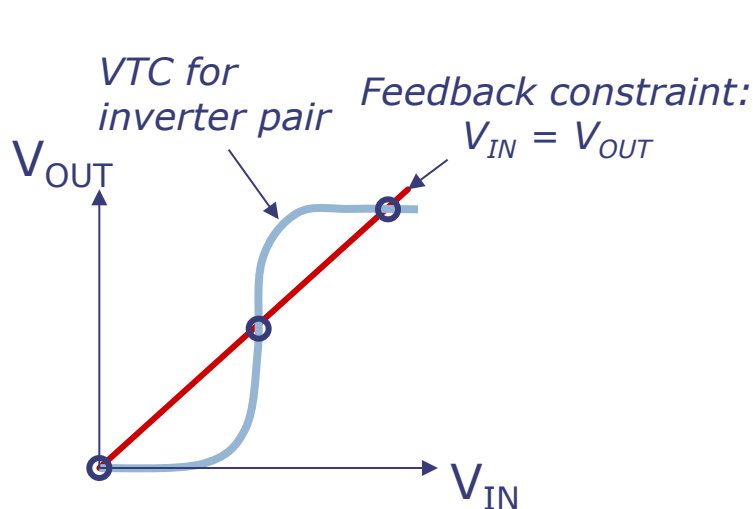

Not affected by noise



Three solutions:

- two end-points are **stable**
- middle point is metastable

We'll get back to this!

D Latch


A simple circuit that can hold state

  

if $C=1$, the value of Q *holds*
 if $C=0$, the value of D *passes* to Q



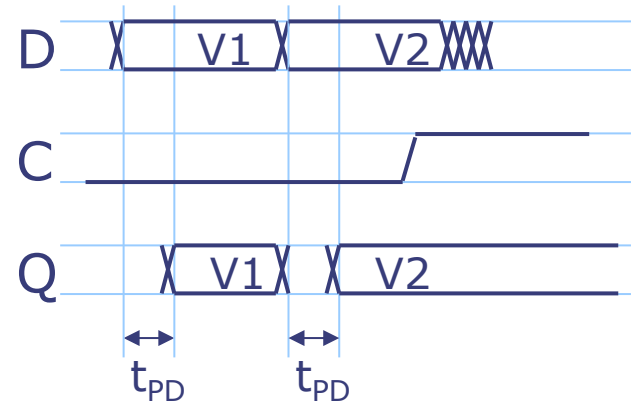
Q^{t-1} represents the value previously held in DL;
 Q^t represents the current value.



C	D	Q^{t-1}	Q^t	
0	0	X	0	} pass
0	1	X	1	
1	X	0	0	} hold
1	X	1	1	

Sequential circuits using D latches?

A terrible idea

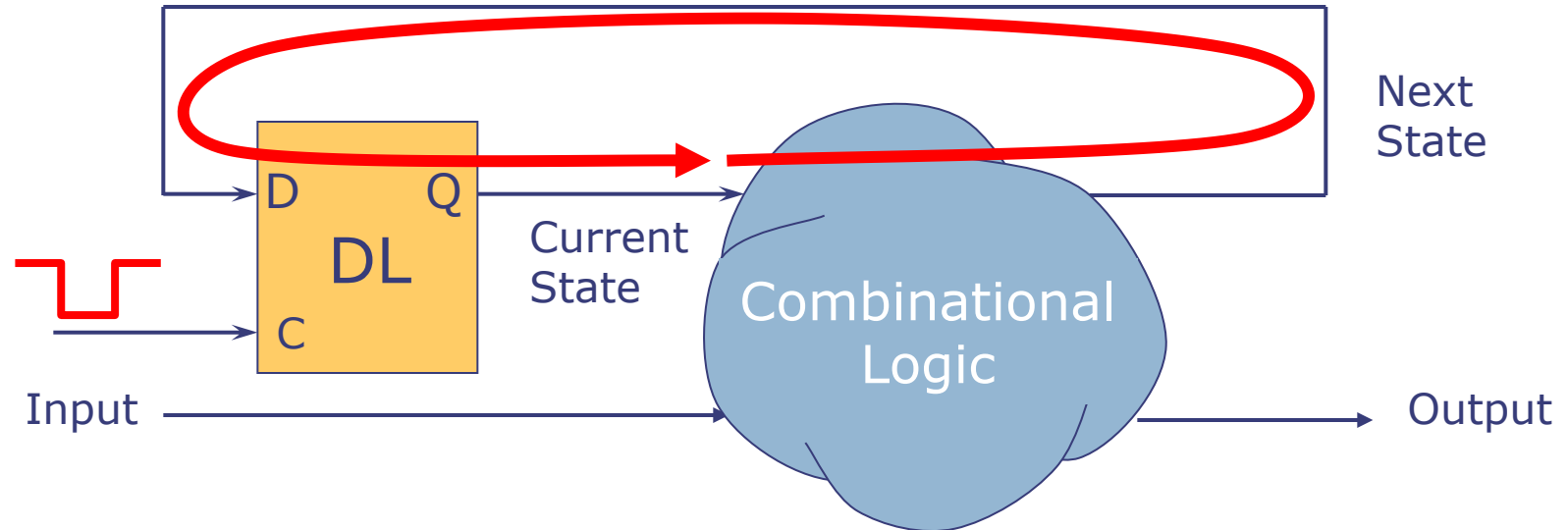


- When $C=0$, D latch passes input to output...
 - Creates a cycle from Q to D!
 - Our combinational logic stops being combinational ☹️
- In practice, very hard to get right: Needs tricky timing constraints on $C=0$ pulse + comb logic

Memory should sample an *instant*, not an *interval*


A Similar Problem...

Gate closed

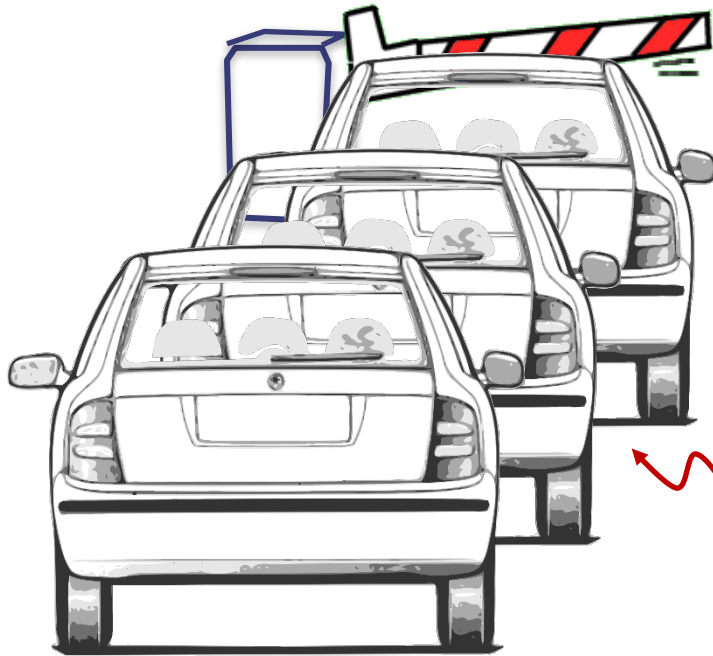


Sequence of values

Gate open

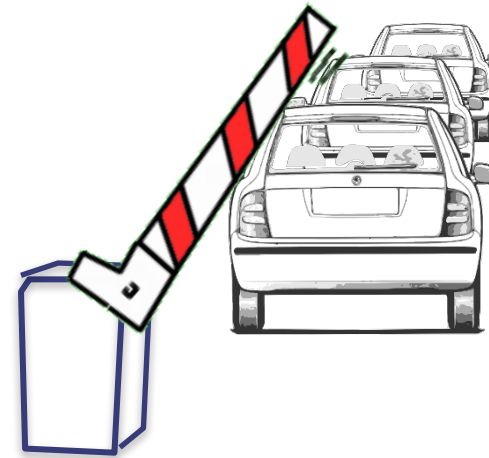

How can we ensure only one car gets through?


Solution: Use two gates!

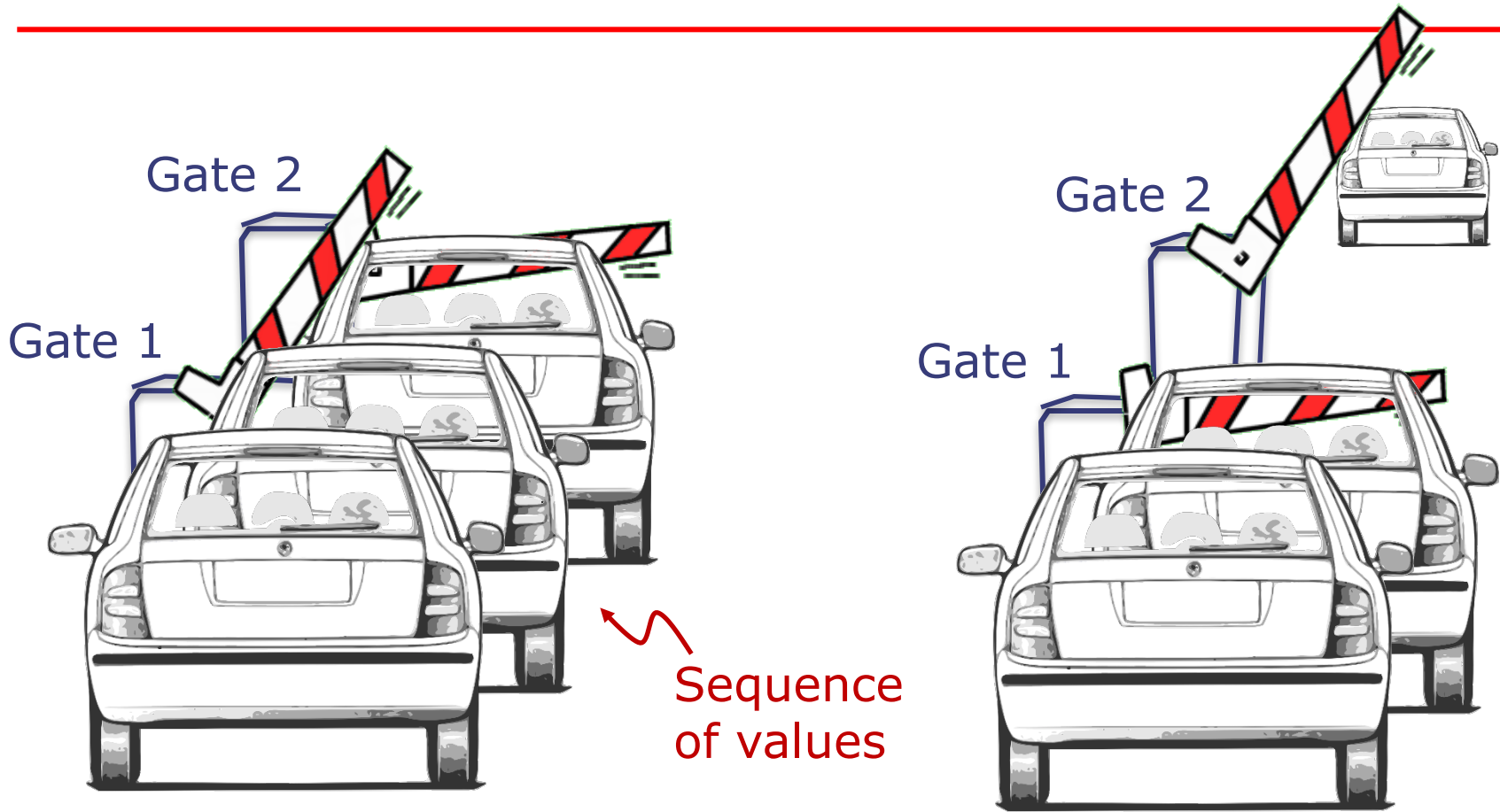

Gate 1: open
Gate 2: closed


Gate 1: closed
Gate 2: open

D Flip-Flop

 


- Two latches driven by inverted C signals, one is always holding, and one is always passing
- How does this circuit behave?
 - $C = 0$: Q^{int} follows the input D, but Q holds its old value

D Flip-Flop

 

- Two latches driven by inverted C signals, one is always holding, and one is always passing
- How does this circuit behave?
 - $C = 0$: Q^{int} follows the input D, but Q holds its old value
 - $C = 1$: Q^{int} holds its old value, but Q follows Q^{int}
 - Q doesn't change when $C=0$ or $C=1$
 - It changes when **C transitions from 0 to 1 (a rising-edge of C)**

D Flip-Flop

 


- Two latches driven by inverted C signals, one is always holding, and one is always passing
- How does this circuit behave?
 - $C = 0$: Q^{int} follows the input D, but Q holds its old value
 - $C = 1$: Q^{int} holds its old value, but Q follows Q^{int}
 - Q doesn't change when $C=0$ or $C=1$
 - It changes when **C transitions from 0 to 1 (a rising-edge of C)**


What happens on a falling edge ($C: 1 \rightarrow 0$)?

D Flip-Flop

An *edge-triggered* storage element


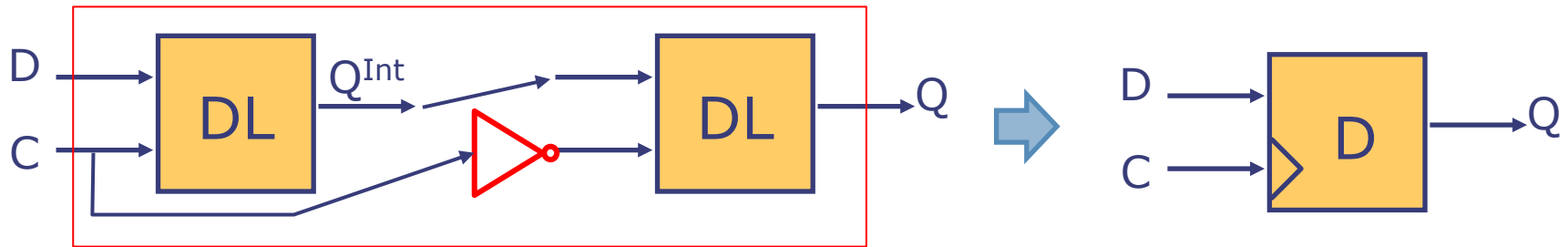


 C changes periodically (a *Clock* signal)




Data is sampled at the rising edge of the clock and must be **stable** at that time

D Flip-Flop Timing

  




- Flip-flop input D should not change around the rising edge of the clock to avoid *metastability*
- Formally, D should be a stable and valid digital value:
 - For at least t_{SETUP} before the rising edge of the clock
 - For at least t_{HOLD} after the rising edge of the clock
- Flip-flop propagation delay t_{PD} is measured from **rising edge of the clock** to **valid output** (CLK \rightarrow Q)

Sequential Circuits using D Flip-Flops

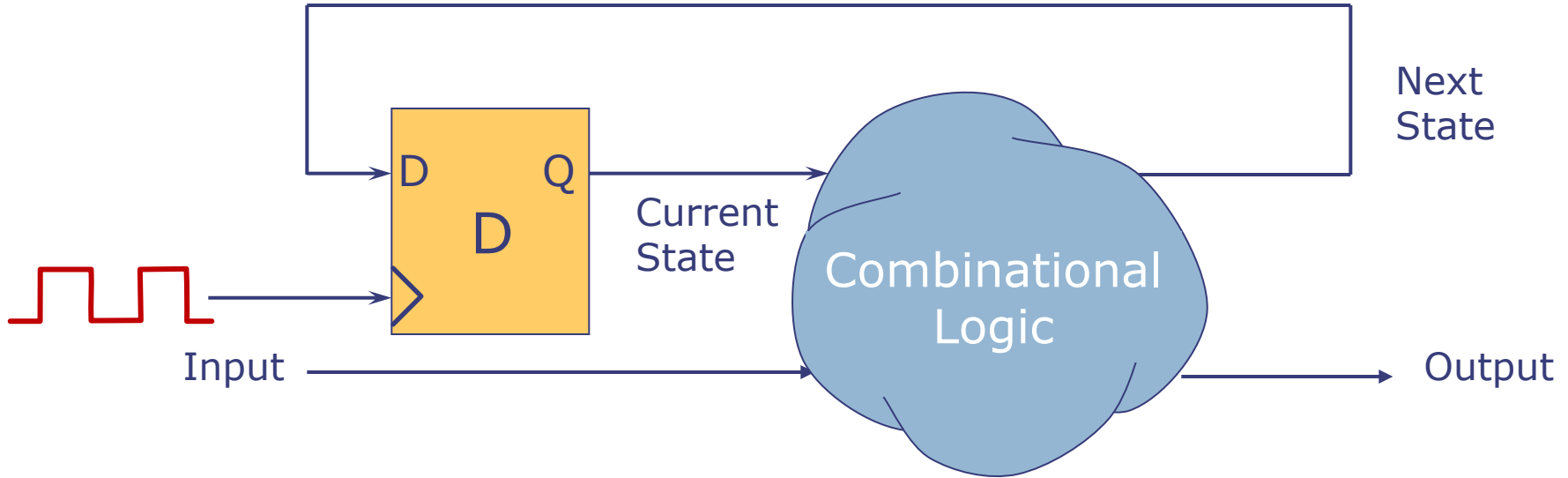

- There is never a combinational cycle between D and Q!
- Works correctly, as long as we meet t_{SETUP} and t_{HOLD}
 - More on this later

D Flip-Flop with Write Enable

  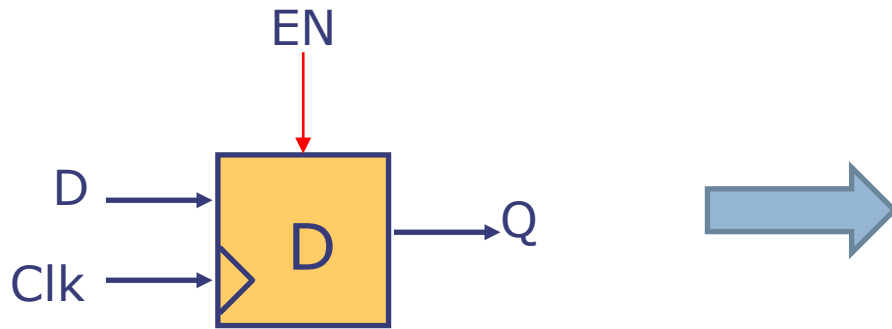

EN	D	Q^t	Q^{t+1}
0	X	0	0
0	X	1	1
1	0	X	0
1	1	X	1


hold

copy input

Data is captured only if EN is on

Transitions happen at **rising edge of the clock**
No need to specify the clock explicitly

How Are Flip-Flops Initialized?

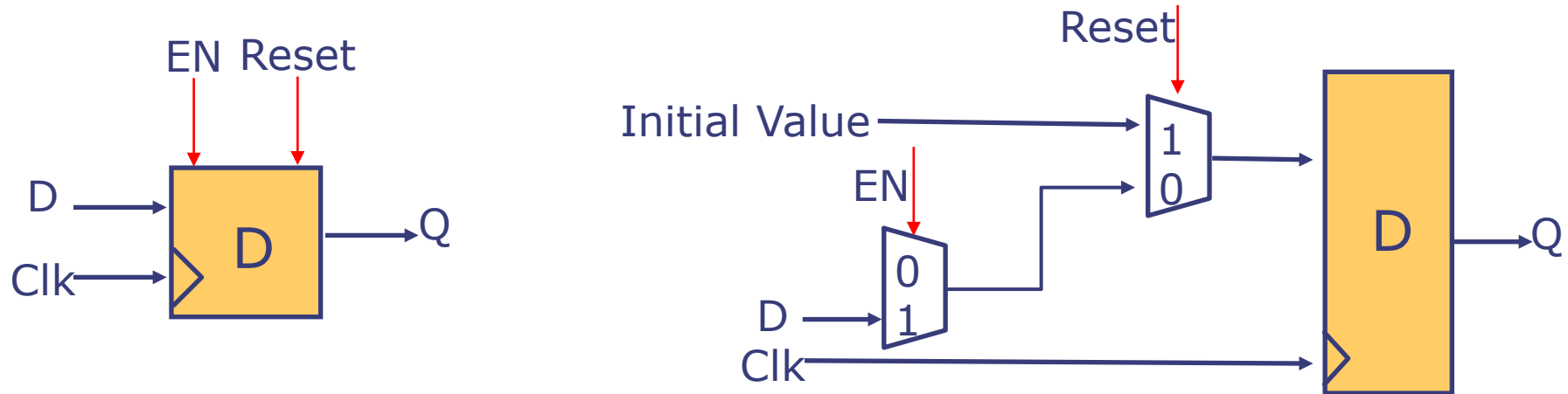


- When $\text{Reset} = 1$, flip flop is set to initial value regardless of value of EN
- When $\text{Reset} = 0$, then it behaves like a D flip-flop with enable

Using D Flip-Flops to Build Sequential Circuits


Synchronous Sequential Circuits

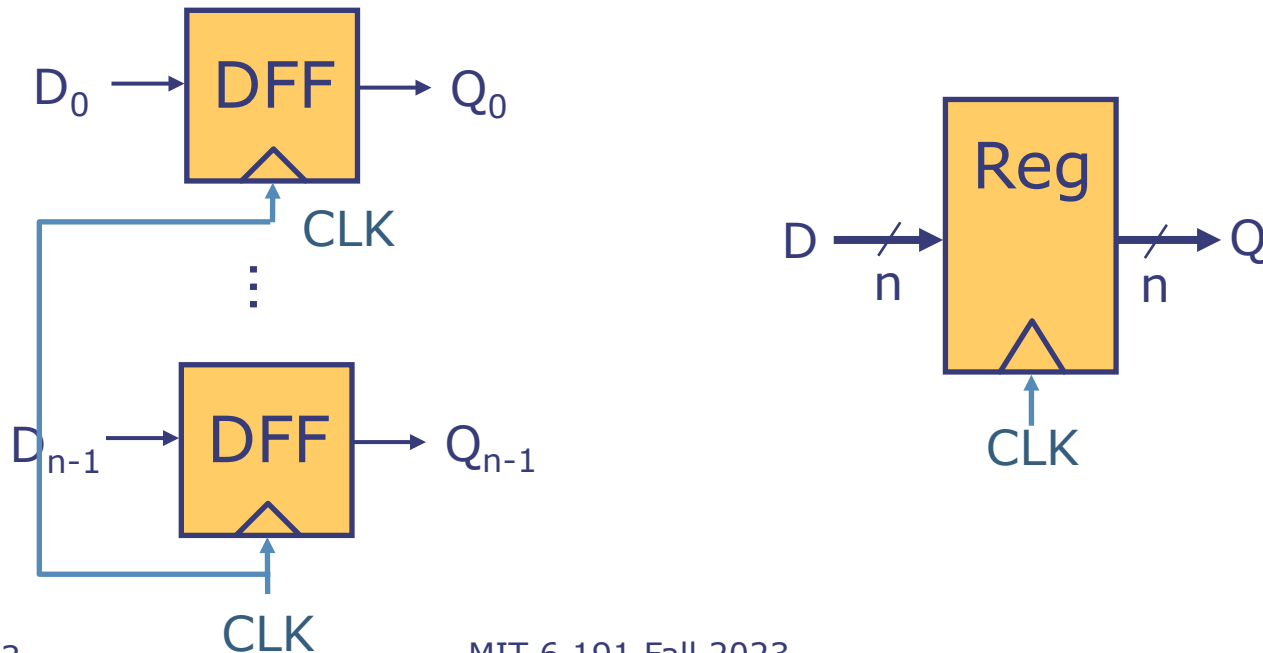- All the D Flip-Flops use the same periodic clock signal
- Register: Group of DFFs
 - Stores multi-bit values
- Registers update their contents simultaneously, at the rising edge of the clock




Synchronous Sequential Circuits

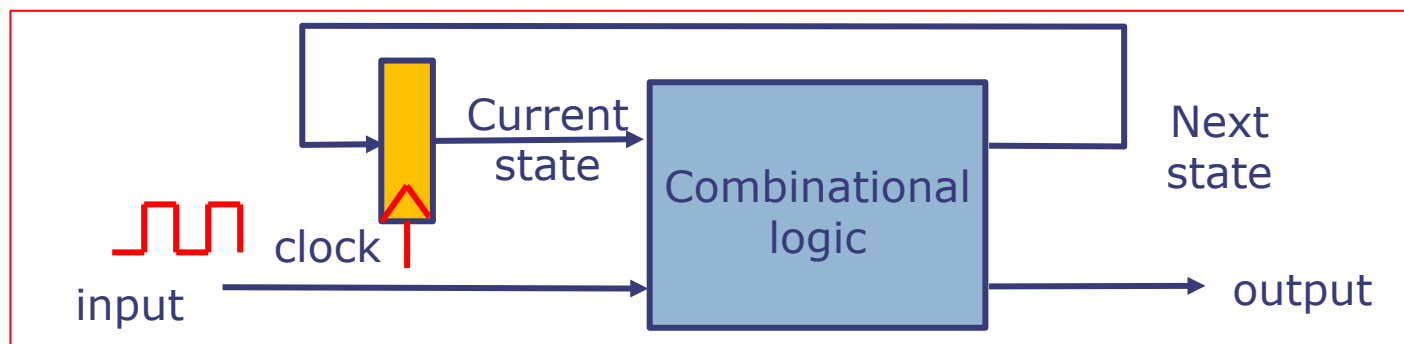- Synchronous sequential circuits: All state kept in registers driven by the same clock
- This allows discretizing time into cycles and abstracting sequential circuits as **finite state machines (FSMs)**
- FSMs can be described with **state-transition diagrams** or truth tables



A Simple Sequential Circuit

 Let's make a digital binary *Combination Lock*:




Specification:

- A 1-bit input (“0” or “1”)
- A 1-bit output (“Unlock” signal)
- UNLOCK is 1 if and only if:
Last 4 inputs were the “combination”: 0110


How many states do we need?

State-Transition Diagram

 

Designing our lock

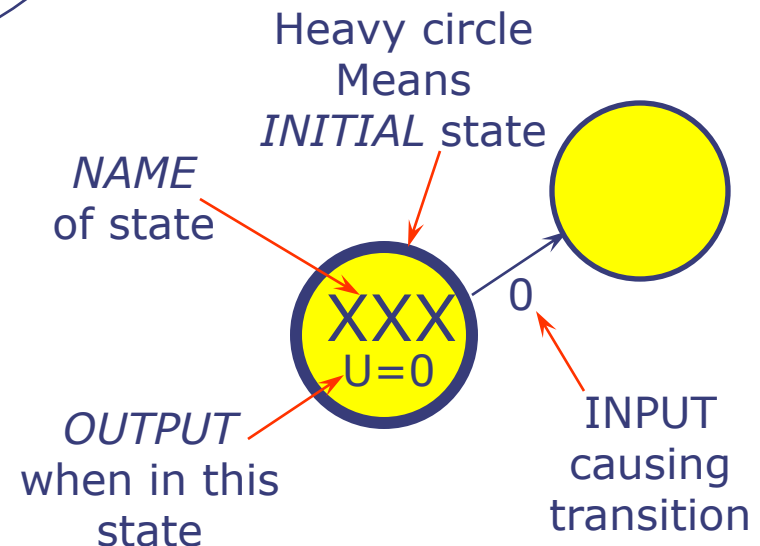- Need an initial state; call it S0.
- Must have a separate state for each step of the proper entry sequence
- Must handle other (erroneous) entries



Valid State-Transition Diagrams

- Arcs leaving a state must be:

(1) **mutually exclusive**


- *For a given input value, can't have two choices*

(2) **collectively exhaustive**

- *Every state must specify what happens for each possible input combination*
- *"Nothing happens" means arc back to itself*

Two-Bit Counter

An Example

 

State-Transition Diagram

$$\begin{aligned}q_0^{t+1} &= \sim inc \cdot q_0^t + inc \cdot \sim q_0^t \\ &= inc \oplus q_0^t\end{aligned}$$

$$\begin{aligned}q_1^{t+1} &= \sim inc \cdot q_1^t + inc \cdot \sim q_1^t \cdot q_0^t + inc \cdot q_1^t \cdot \sim q_0^t \\ &= \sim inc \cdot q_1^t + inc \cdot (q_1^t \oplus q_0^t)\end{aligned}$$

$$\text{Output} = \text{current state} = q_1 q_0$$

Current State			Next State	
inc	q_1^t	q_0^t	q_1^{t+1}	q_0^{t+1}
0	0	0	0	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	1
1	0	0	0	1
1	0	1	1	0
1	1	0	1	1
1	1	1	0	0


Two-Bit Counter Circuit

Using D flip-flops

$$q_0^{t+1} = \sim inc \cdot q_0^t + inc \cdot \sim q_0^t$$
$$q_1^{t+1} = \sim inc \cdot q_1^t + inc \cdot (q_1^t \oplus q_0^t)$$



- Use two D flip-flops with *reset* and *enable* to store q_0 and q_1
- The state only changes when inc is 1. Let's connect inc to **EN** and simplify the equations
- Output is q_1q_0
- Set Initial Value of both flip-flops to 0 (initial state: 00)
 - Loaded when Reset = 1
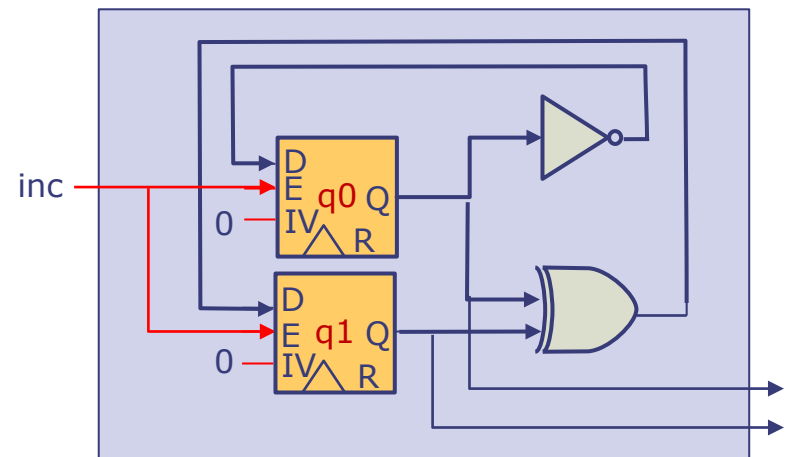
$$\left. \begin{aligned} q_0^{t+1} &= \sim q_0^t \\ q_1^{t+1} &= q_1^t \oplus q_0^t \end{aligned} \right\} inc=1$$





Timing Constraints in Sequential Circuits

Recap: D Flip-Flop Timing

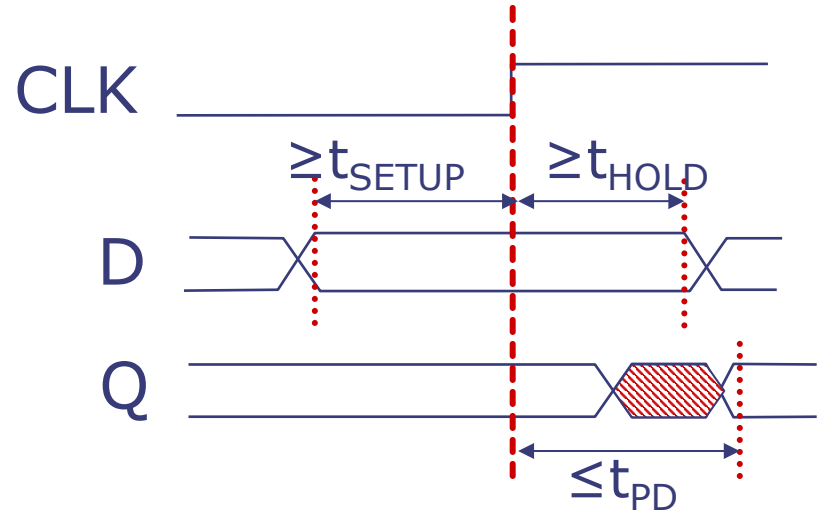 


- Flip-flop input D should not change around the rising edge of the clock to avoid *metastability*
- Formally, D should be a stable and valid digital value:
 - For at least t_{SETUP} before the rising edge of the clock
 - For at least t_{HOLD} after the rising edge of the clock
- Flip-flop propagation delay t_{PD} is measured from rising edge of the clock to valid output (CLK \rightarrow Q)

Single-clock Synchronous Circuits

 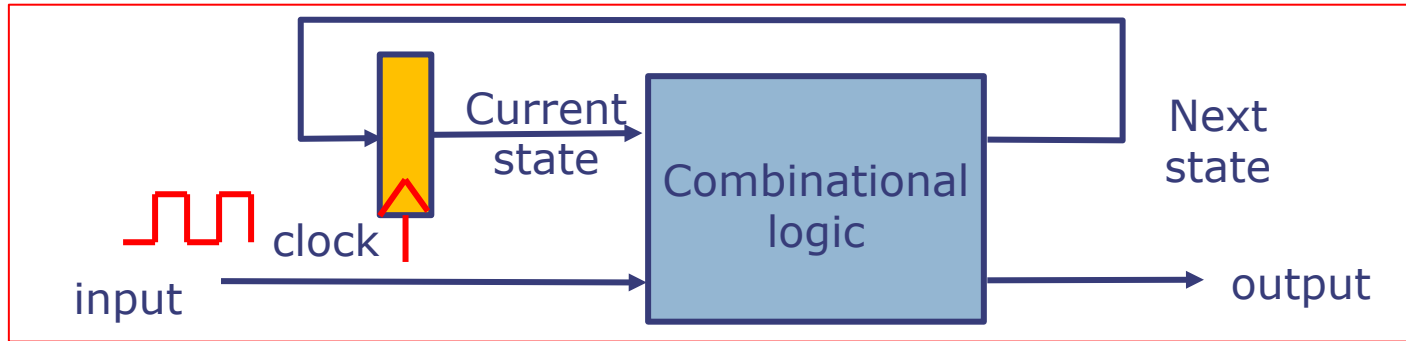

Need to analyze
the timing of each
register-to-register path

Meeting the Setup-Time Constraint


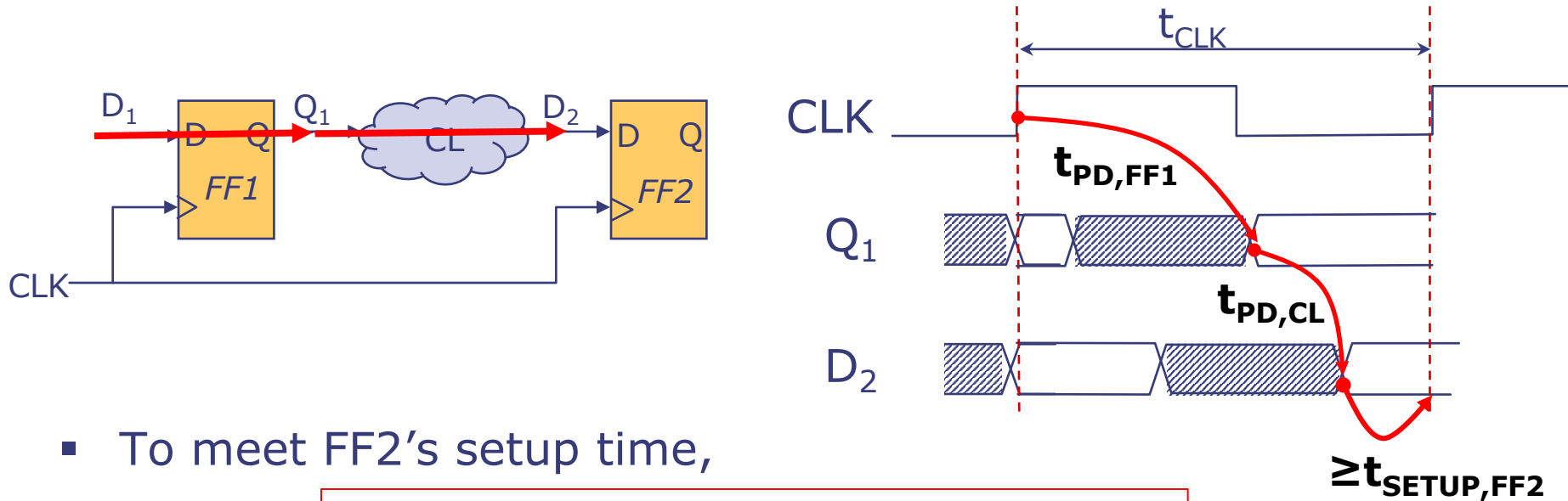


- To meet FF2's setup time,

$$t_{CLK} \geq t_{PD,FF1} + t_{PD,CL} + t_{SETUP,FF2}$$

- The **slowest** register-to-register path in the system determines the clock;
- Equivalently, a given register technology and clock limit the amount of combinational logic between registers

Meeting the Hold-Time Constraint

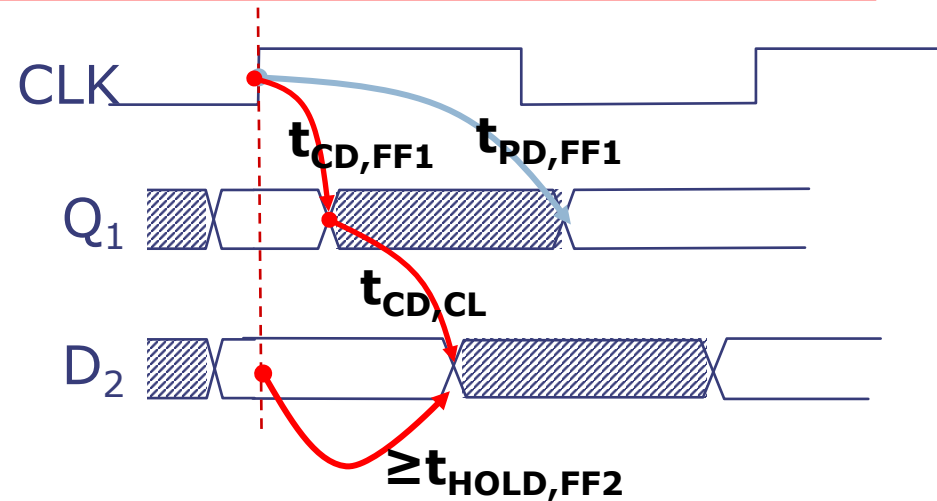 

- Hold time (t_{HOLD}) constraint of FF2 may be violated if D₂ changes too quickly
- Propagation delay (t_{PD}), the upper bound on time from valid inputs to valid outputs, does not help us analyze hold time!
- *Contamination delay* (t_{CD}) is the lower bound on time from input-to-output transition (invalid input to invalid output)
- To meet FF2's hold-time constraint


$$t_{CD,FF1} + t_{CD,CL} \geq t_{HOLD,FF2}$$

Tools may need to add logic to fast paths to meet t_{HOLD}

Timing Summary

- For a sequential circuit to work properly, we must guarantee that the **setup time** and **hold time** constraints of every register will always be satisfied.
- The **setup time** constraint is affected by both the logic in the circuit *and* the clock period. To fix violations, either:
 - Change the logic to be faster (lower t_{PD})
 - Change the clock to be slower (higher t_{CLK})
- The **hold time** constraint is affected *only* by the logic in the circuit.
 - Changing the clock period will not fix violations.
 - Sum of contamination delays must be greater than the register hold time, otherwise the circuit won't work.
- If hold time is satisfied, then the fastest clock period can be set as the **maximum sum of the propagation delays plus setup time** across all register-to-register paths.

Sequential Circuit Timing Example

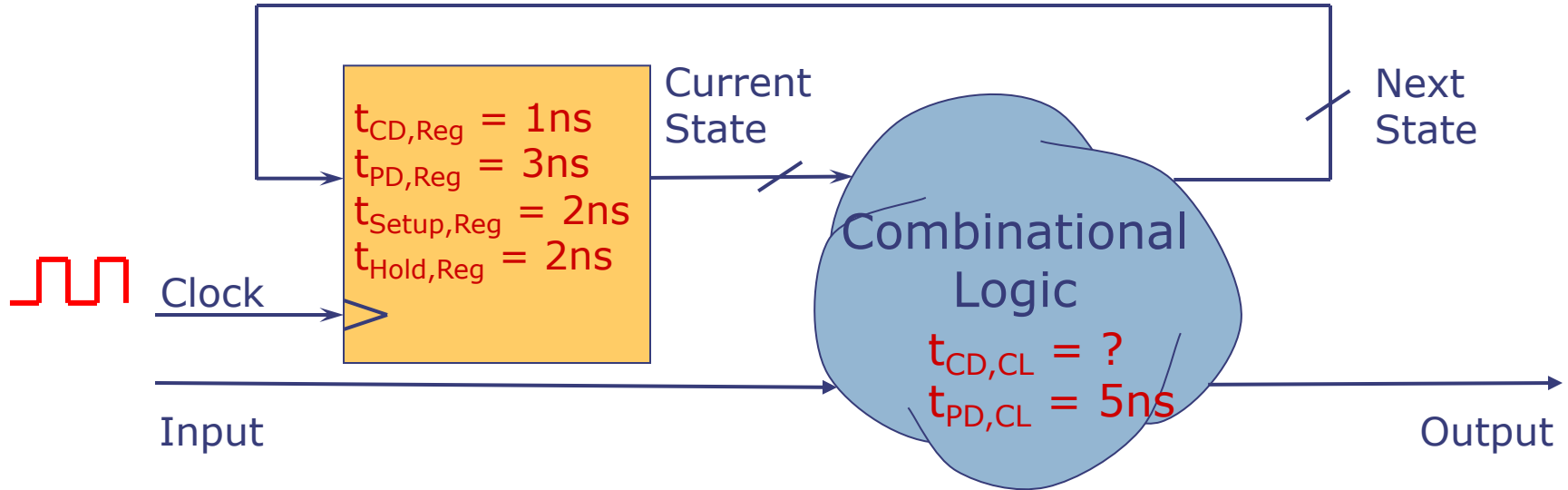

Questions:

- Constraints on t_{CD} for the logic?

$$t_{CD,Reg} (1 ns) + t_{CD,CL} (?) \geq t_{Hold,Reg} (2 ns)$$

$$t_{CD,CL} \geq 1 ns$$

- Minimum clock period?

$$t_{CLK} \geq t_{PD,Reg} + t_{PD,CL} + t_{Setup,Reg} = 10ns$$

Thank you!

Next lecture:
Sequential logic in Minispec