

Intro to Verilog

Kosi Nwabueze <kosinw@mit.edu>


Spring 2026




What is Verilog?

Verilog is a *hardware description language* — it describes digital circuits, not software programs.

 
When you write **Verilog**, you are specifying digital logic behavior: logic gates, flip-flops, and latches.



Verilog
(synthesizable)

 

Verilog
(simulatable)

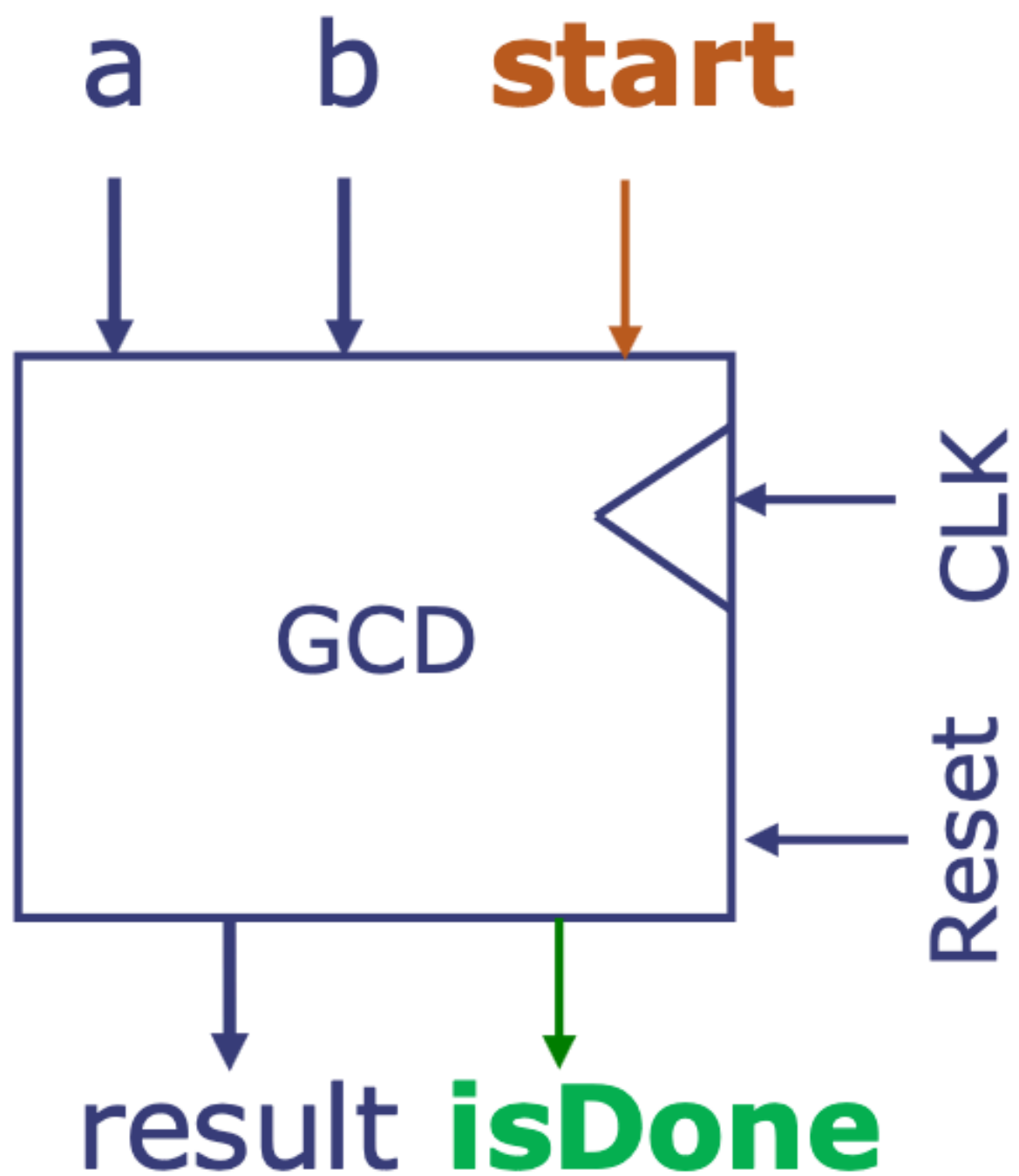


```

1  module GCD (
2      input  logic          clk, rst, start,
3      input  logic [31:0] a, b,
4      output logic [31:0] result,
5      output logic          isDone
6  );
7      // TODO: implement me
8  endmodule

```

 Modules are the unit of ***abstraction*** in a circuit.



```


1  module GCD (
2      input  logic          clk, rst, start,
3      input  logic  [31:0] a, b,
4      output logic  [31:0] result,
5      output logic          isDone
6  );
7      // TODO: implement me
8  endmodule

```

Input / output ports


Inputs ports drive the circuit; **output ports** carry results.

(as combinational logic)

 

```
1 logic a;  
2 logic b;  
3  
4 assign c = a + b;
```

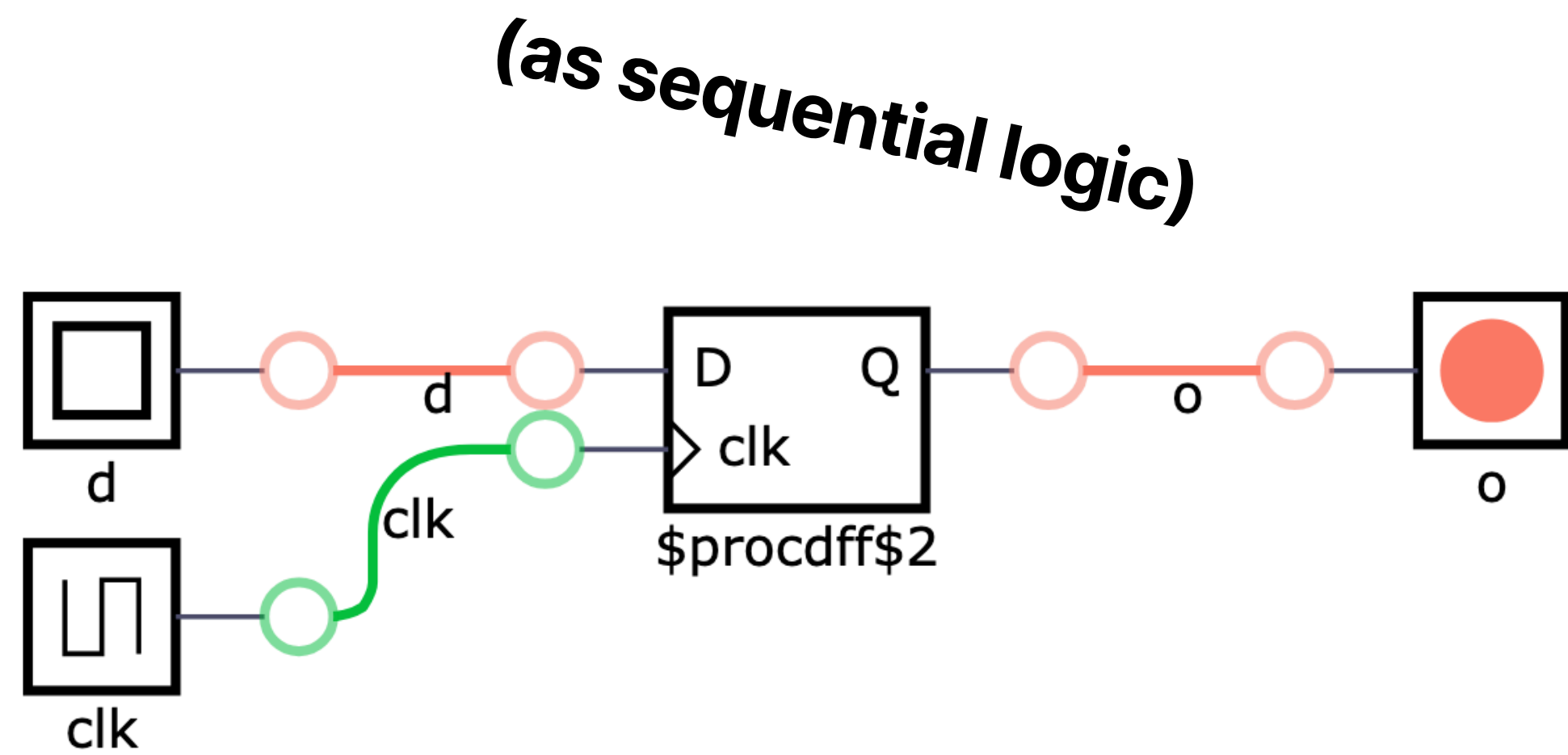Signals are declared using `logic`.
The **usage** determines its synthesis **behavior**.



```
1  logic d;  
2  logic clk;  
3  logic o;  
4  
5  always_ff @(posedge clk) begin  
6      o <= d;  
7  end
```

Signals are declared using `logic`.
The **usage** determines its synthesis **behavior**.

```
1  logic a;           // create one bit variable
2  logic [3:0] b;     // create four bit variable
3  logic [11:0] c,d,e; // create several 12 bit variables
```

Signals can be declared with flexible size in hardware.
Sizing is specified from leftmost bit to rightmost.

```
1  logic a;  
2  wire b;  
3  reg c;
```

Signals may also be declared with `wire` and `reg`.
For most cases, prefer using `logic`.

```
1  logic [7:0] in1, in2;
2  logic [7:0] a, b;
3
4  assign a = in1 ^ in2;
5
6  always_comb begin
7      b = in1 + in2;
8  end
```

Signals assigned to within combinational logic use ***blocking assignment*** (=) w/ assign or always_comb.

```
1  logic [7:0] a;  
2  
3  always_ff @(posedge clk) begin  
4      a <= b + c;  
5  end
```

Signals assigned to within sequential logic use ***non-blocking assignment*** (<=) in an always_ff.

```
1  logic [7:0] a;
2
3  always_ff @(posedge clk) begin
4      a <= b + c;          sensitivity list
5  end
```

Sensitivity lists describes when the procedural block fires. The block fires when at least one of the signals changes (posedge/negedge).

(below are bad examples)

```
1  always_ff @(posedge clk) begin
2      a = b;
3      c = a;
4  end
5
6  always_ff @(posedge clk) begin
7      addition_result = input + 2'd2;
8      xor_result <= input & addition_result;
9      output = xor_result;
10 end
```

In general, separate **blocking** and **non-blocking** assignments into `always_comb` and `always_ff` blocks.

```
1  always_comb begin
2      out = 32'h0;
3      if (enable) begin
4          case (mode)
5              2'b00: out = a + b;
6              2'b01: out = a - b;
7              2'b10: out = a ^ b;
8              default: out = a;
9          endcase
10     end
11 end
12
```

Conditionals are used for *data-dependent* behavior in combinational logic. Assignment within a conditional will be synthesized as a **multiplexer**.

```
1 // --- sized literals ---
2 logic [31:0] word = 32'hdeadbeef;
3 logic [3:0] nibble = 4'b1010;
4 logic [7:0] byte = 8'd255;
```

Sized literals are of the form size (in bits), base (hex, decimal, or binary), and literal.

```
1 // --- bit slice ---  
2 logic [31:0] instr = 32'h00c58533;  
3 logic [11:0] imm_i = instr[31:20]; // 12'h00c
```

Bit-slicing enables accessing a subset of the bits from a signal (from MSB to LSB).

```
1 // --- concatenation ---
2 logic [15:0] hi = 16'h1234;
3 logic [15:0] lo = 16'h5678;
4 logic [31:0] combined = {hi, lo}; // 32'h12345678
```

Concatenation allows combining multiple signals together by sequentially combining their bits.

```
1 // --- bitwise ops (operate bit-by-bit on vectors) ---
2 logic [7:0] a = 8'h0f;
3 logic [7:0] b = 8'h33;
4 logic [7:0] bw_and = a & b;
5 logic [7:0] bw_or = a | b;
6 logic [7:0] bw_xor = a ^ b;
7 logic [7:0] bw_not = ~a;
```

Bitwise operations apply Boolean functions bit-by-bit on given bitvectors.

```
1 // --- logical ops (treat vectors as "true if nonzero") ---
2 logic enable = 1'b1;
3 logic ready  = 1'b0;
4 logic go     = enable && !ready;
```

Logical operations allow Boolean operations on bitvectors where they are true only if nonzero.